

## TODAY'S STANDARD

*Electrical Energy & Circuits*

Demonstrate and describe how electrical energy travels in a closed path that can produce light and thermal energy.

## TODAY'S LEARNING GOAL

*Electrical Energy & Circuits*

# I can...

build a closed circuit that  
lights a bulb or makes  
heat.

## TODAY'S LEARNING GOAL

*Electrical Energy & Circuits*

# I can...

trace the path electricity takes from the battery and back again.

## TODAY'S LEARNING GOAL

*Electrical Energy & Circuits*

# I can...

explain why a circuit has to be complete for electrical energy to flow.

## TODAY'S LEARNING GOALS

*Electrical Energy & Circuits***I can...**

- build a closed circuit that lights a bulb or makes heat.
- trace the path electricity takes from the battery and back again.
- explain why a circuit has to be complete for electrical energy to flow.